

ROM MACRO DESIGN

Abstract - We propose a 1024 bits read only memory (ROM) with dynamic column sources, which enable us to achieve the high speed and the relative low power consumption. ROM macro using 180nm CMOS bulk technology realizes 0.814ns read access time at TT25 / 1.8V / 100MHz.

I. INTRODUCTION

The macro consists of ROM, decoders, muxs, DFFs, SAs and the timing control. Its widths and lengths are very important. If we does not choose proper sizes, the circuit will not work.Finally, We simply use 11 inputs to produce wanted signals.

Due to regulations, the access time of the ROM Macro need to smaller than 5ns. The statistics of the access time in different corners are showed in the Table 1.Overall, the power supply is 1.8V and the macro size is 12355 μm^2 . We measure the power consumption and the delay time corresponding five corners at TT25°C, SF25°C, FS25°C, SS25°C and FF25°C respectively. Obviously, we satisfy the need.

TABLE I
THE STATISTICS OF MACRO

Process	180nm cmos
Macro size	12355 μm
power_presim at TT25°C	586 μw
power_postsim at TT25°C	945.7 μw
access time_presim at TT25°C	2.576ns
access time_postsim at TT25°C	2.963ns
access time_presim at SF25°C	4.5316ns
access time_presim at FS25°C	2.267ns
access time_presim at SS25°C	3.392ns
access time_presim at FF25°C	2.628ns

A. The block diagram of ROM macro

The functional block diagram is shown in figure 1. Following function blocks contains : Timing control, Decoder, ROM, D flip-flop, Sense amplifier and additional output Latch.

(1)*Timing Control*: Making a pulse by differentiating the input into two inputs of a AND gate, one of which are connected to an inverter chain. While requiring two circuits above to make WL_EN and SA_EN, the adjustment of the delay and the width of the pulse results to the extra requirement of inverter chains.

(2)*Decoders*: Using a 6 to 64 decoder selects the rows of ROM and using two 8 to 1 mux selects the columns of ROM. That is, we can view the ROM as 1024-square division. Decoders choose a aquare from the ROM, which depends on the output of decoders.

(3)*ROM*: It contains datas which are setted in advance.

(4)*MUX*: Using two 8 to 1 mux selects the columns of ROM. Muxs are controlled by the 3 to 8 decoder.

(5)*Sense Amplifier*: Comparing the bit line voltage with Vref to sense the data.

(6)*DFF*: Sending the input A[8:0] to the X and Y decoder, which is controlled by the clock.

(7)*Precharge*: Precharge BL to VDD every cycle when clk is low level for avoiding read disturbs.

(8)*Latch*: Keep the output signal from sense amplifier to next CLK rising edge.

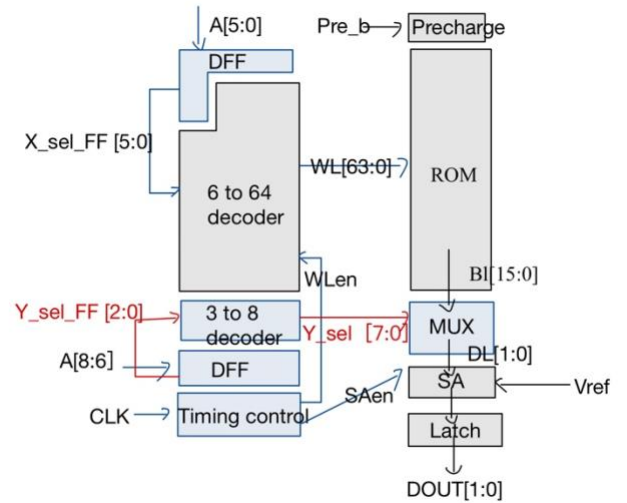


Fig. 1 ROM macro block diagram

(1) *Timing Control:*

Total timing control circuit:

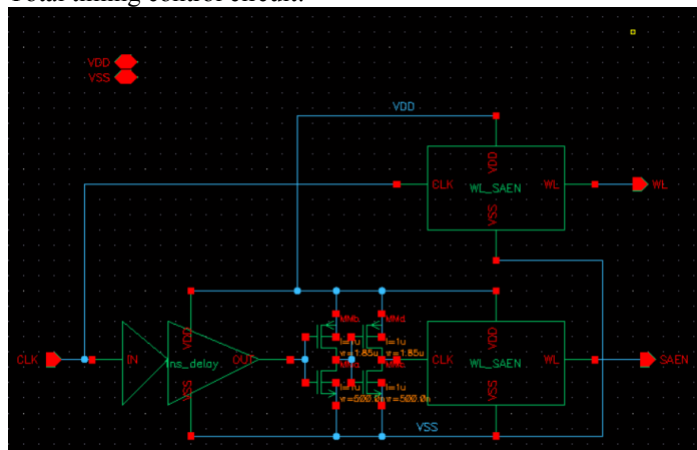


Fig. 2-1 Total timing control circuit

 


Fig. 2-2 The WL_SAEN circuit

Inverter chain in the WL SAEN circuit:

 


Fig. 2-3 Inverter chain in the WL_SAEN circuit

AND2:

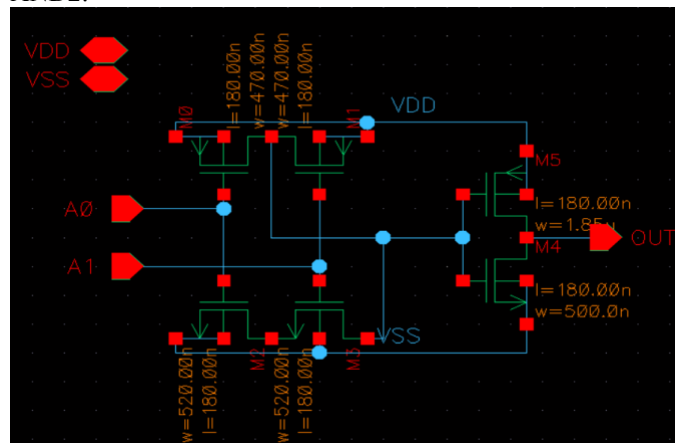


Fig. 2-4 AND2 gate

(2) *Decoders:*

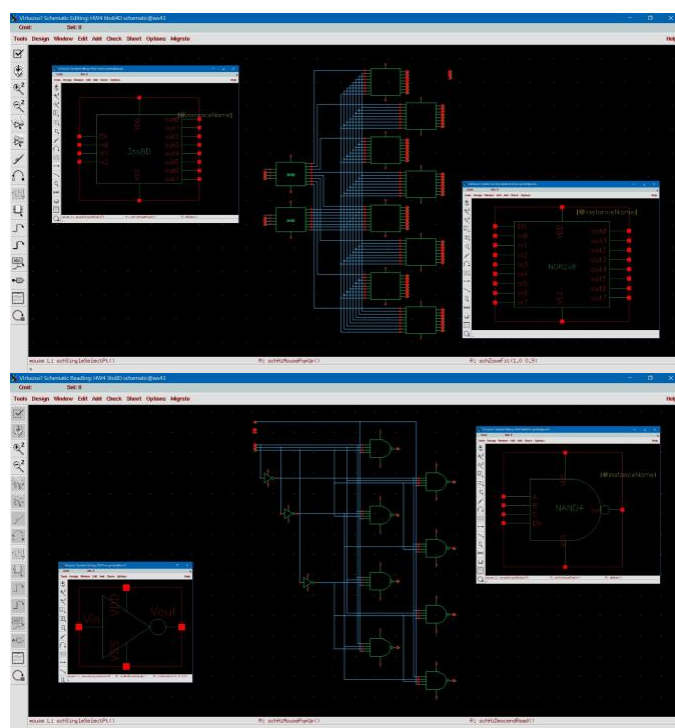




Fig. 2-5~2-9 Decoders

(3)ROM:

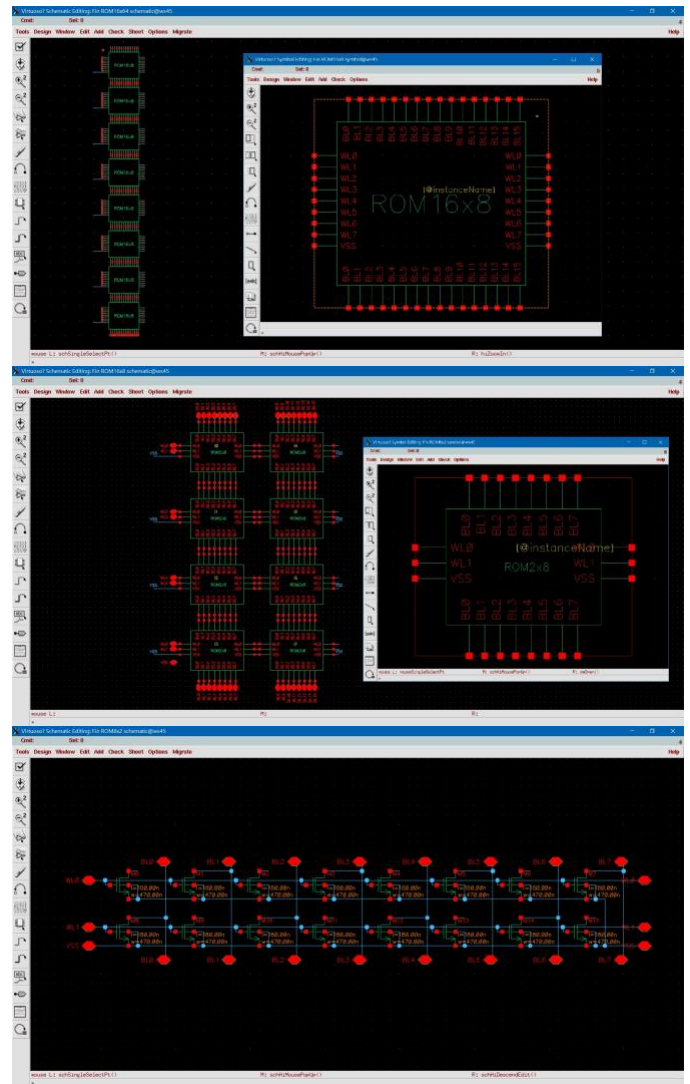
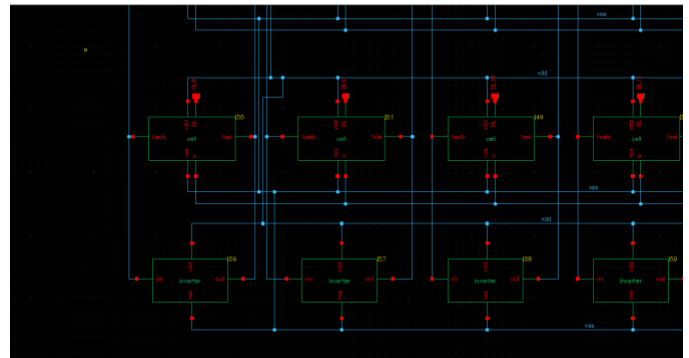



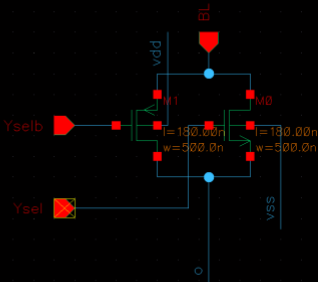


Fig. 2-10~2-12 ROM

(4)MUX:



vdd  vss  *
 o 




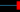

 
Yselb   M1
 l=180.00n
 w=500.0n
 Ysel   M0
 l=180.00n
 w=500.0n
 vdd
 vss
 O

Fig. 2-13~2-14 MUX:

The diagram illustrates a 2x2 MIMO system with two identical transmitter and receiver chains. Each transmitter chain consists of a 100mW PA, a 100pF capacitor, a 100nH inductor, and a 100pF capacitor. Each receiver chain consists of a 100pF capacitor, a 100nH inductor, and a 100pF capacitor. The system is powered by VDD and GND.

Fig. 2-15 Sense Amplifier

[illegible]

Fig. 2-16 DFF

[illegible]

Fig. 2-17 Precharge

[illegible]

Fig. 2-18 Latch

However, we want to figure out the worst case so we need to run our circuits in different situations. Apparently, the worst case is in SS corner. Detailed statistics are showed in table2.

 


Fig. 3 The wavefrom of ROM mcaro in TT25°C

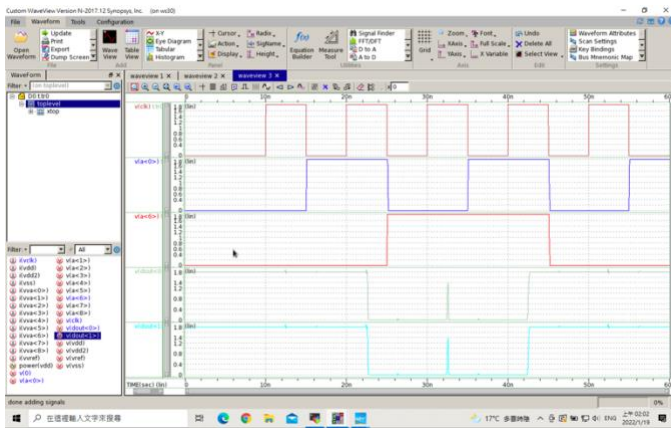


Fig. 3-1 The waveform of ROM macro in SS25°C

 


Fig. 3-4 The waveform of ROM macro in FS25°C

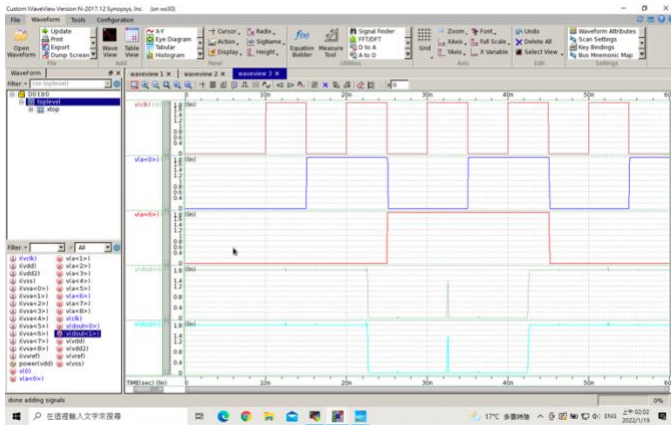


Fig. 3-2 The waveform of ROM macro in FF25°C

 


Fig. 3-3 The waveform of ROM macro in SF25°C

TABLE 2
THE STATISTICS OF MACRO

corners	average power	access time
TT25°C	586μw	2.576ns
SS25°C	856.1μw	4.5316ns
FF25°C	612.94μw	2.267ns
SF25°C	719.7μw	3.392ns
FS25°C	578.9μw	2.628ns

II. IMPLEMENTATION

A. The layout of ROM macro

After running presim, we start to draw the layout of circuits. The figure4-1 is the completed layout.

 


Fig. 4-1 The completed layout of ROM macro

 


Fig. 4-2 The area of ROM macro

B. waveforms postsim in TT25°C

 


Fig. 5 The waveform of ROM macro in TT25°C

corners	average power	access time
TT25°C	945.7μw	2.963ns

C. Compare the result of postsim with presim

The Average power or the access time, the statistics of postsim will be bigger than presim. It makes sense because we use lots of metals when drawing the layout. Moreover, we can find that the waveform of presim is smoother than postsim. It is easy to understand because parasitic resistances and capacitances play a vital role in postsim.

IV. PROBLEMS HAVE CONQUERED

First of all, when we have to design the important part—Timing control, there are several problems such as the exact delay time. If we do not choose proper sizes, the circuit will not work. As a result, the sizes of other parts are determined at first. Then, using unknown input signals such as wlen and saen to perform to check whether the circuits will work or not.

The solution of the above problem is to adjust the length of inverter chain. However, when we do this, another problem has arisen. In TT corner, we can meet the spec but we cannot meet in SS corner. It is because sense enable arrives sense amplifier earlier than data line, which leads to incorrect sensing. Therefore, we try to adjust the length of inverter chain to increase the delay of sense enable so that we can meet the spec.

REFERENCES

- [1] Yukiko Umemoto, “28 nm 50% Power-Reducing Contacted Mask Read Only Memory Macro With 0.72-ns Read Access Time Using 2T Pair Bitcell and Dynamic Column Source Bias Control Technique” IEEE TRANSACTIONS ON VERY LARGE SCALE INTEGRATION (VLSI) SYSTEMS, VOL. 22, NO. 3, MARCH 2014.